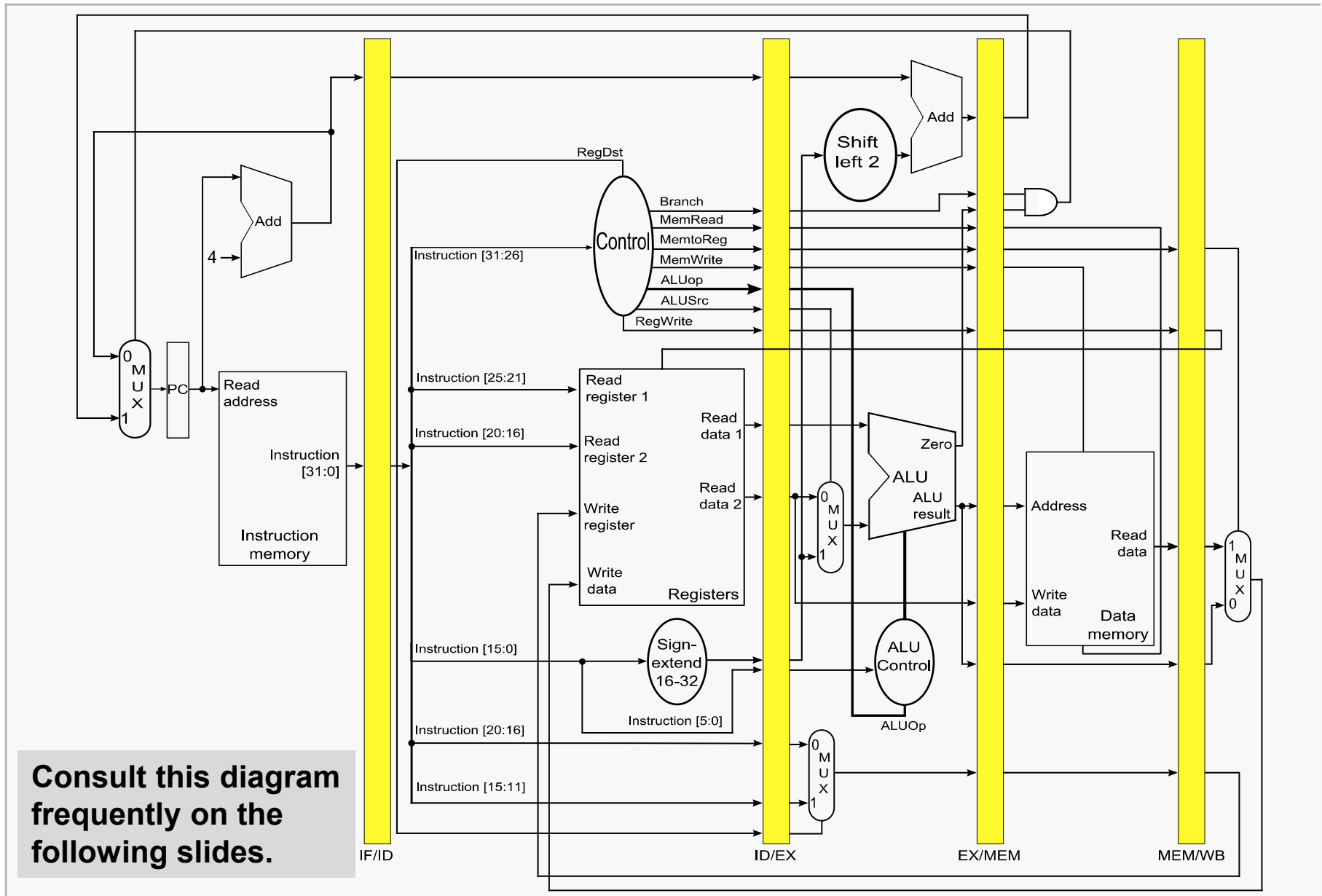


Pipelined Control with Interstage Buffers

Pipeline Control 1



Recall that we must ensure that each control signal “travels with” the instruction to which it applies.

The interstage buffers provide support for this synchronization.

We need to determine which signals each interstage buffers must store.

The key is to determine to which stage a signal must be passed, then make sure it reaches that state in synchronization with the correct instruction.

The Control module sets control signals during the Instruction Decode stage.

The ALUSrc signal must be applied to the multiplexor during the Execute stage, since that is when the corresponding instruction will need for the correct operand to be selected.

Suppose the instruction is fetched on clock cycle N , then:

| cycle | actions |
|---------|--|
| $N + 1$ | instruction enters ID stage; ALUSrc is set |
| $N + 2$ | instruction enters EX stage; ALUSrc is needed at multiplexor |

So, we must store the ALUSrc signal in the ID/EX interstage buffer during clock cycle $N + 1$ when ALUSrc is set, and then read it from the buffer at the beginning of clock cycle $N + 2$ and pass it to the multiplexor.

The Control module sets control signals during the Instruction Decode stage.

The **RegWrite** signal must be applied to the register file during the **WriteBack** stage, since that is when the data produced by the corresponding instruction will reach the register file.

Suppose the instruction is fetched on clock cycle N , then:

| cycle | actions |
|---------|--|
| $N + 1$ | instruction enters ID stage; RegWrite is set |
| $N + 2$ | instruction enters EX stage; RegWrite is not needed yet |
| $N + 3$ | instruction enters MEM stage; RegWrite is not needed yet |
| $N + 4$ | instruction enters WB stage; data is ready to write; data and RegWrite are needed at the register file |

So, we must pass the **RegWrite** signal to the ID/EX interstage buffer, then on to the EX/MEM interstage buffer, and then to the MEM/WB interstage buffer, and finally back to the register file.

Control Signals Grouped by Stages

Pipeline Control 5

| Instruction | Execution/address calculation stage control lines | | | | Memory access stage control lines | | | Write-back stage control lines | |
|-------------|---|--------|--------|--------|-----------------------------------|----------|-----------|--------------------------------|-----------|
| | RegDst | ALUOp1 | ALUOp0 | ALUSrc | Branch | Mem-Read | Mem-Write | Reg-Write | Memto-Reg |
| R-format | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| lw | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 |
| sw | X | 0 | 0 | 1 | 0 | 0 | 1 | 0 | X |
| beq | X | 0 | 1 | 0 | 1 | 0 | 0 | 0 | X |


pass to EX stage

pass to MEM stage

pass to WB stage


Control Signal Forwarding

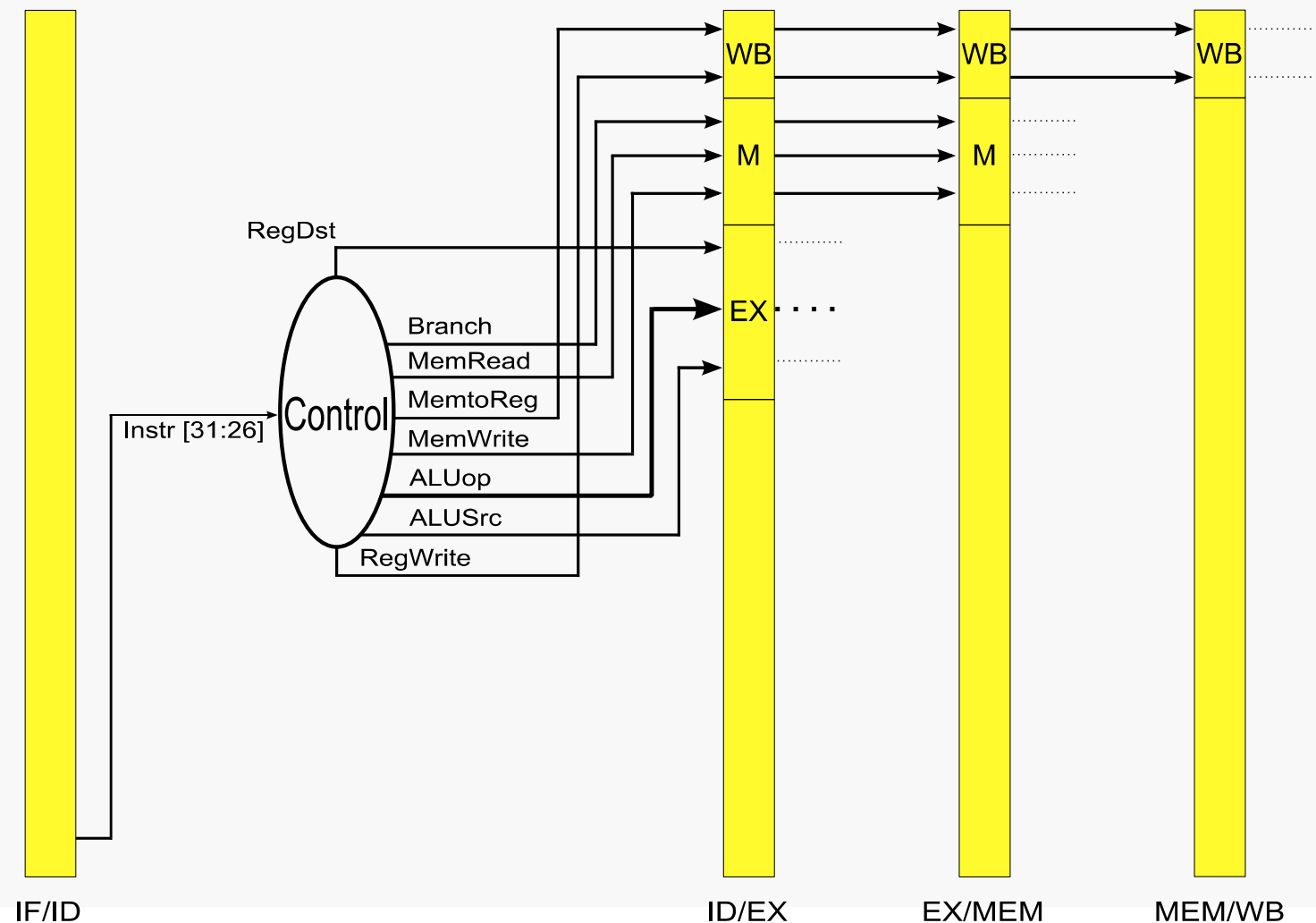Control signals derived from instruction opcode, as before.
Passed synchronously to the appropriate pipeline stage before being applied.



Pipelined Control Overview


Pipeline Control 7

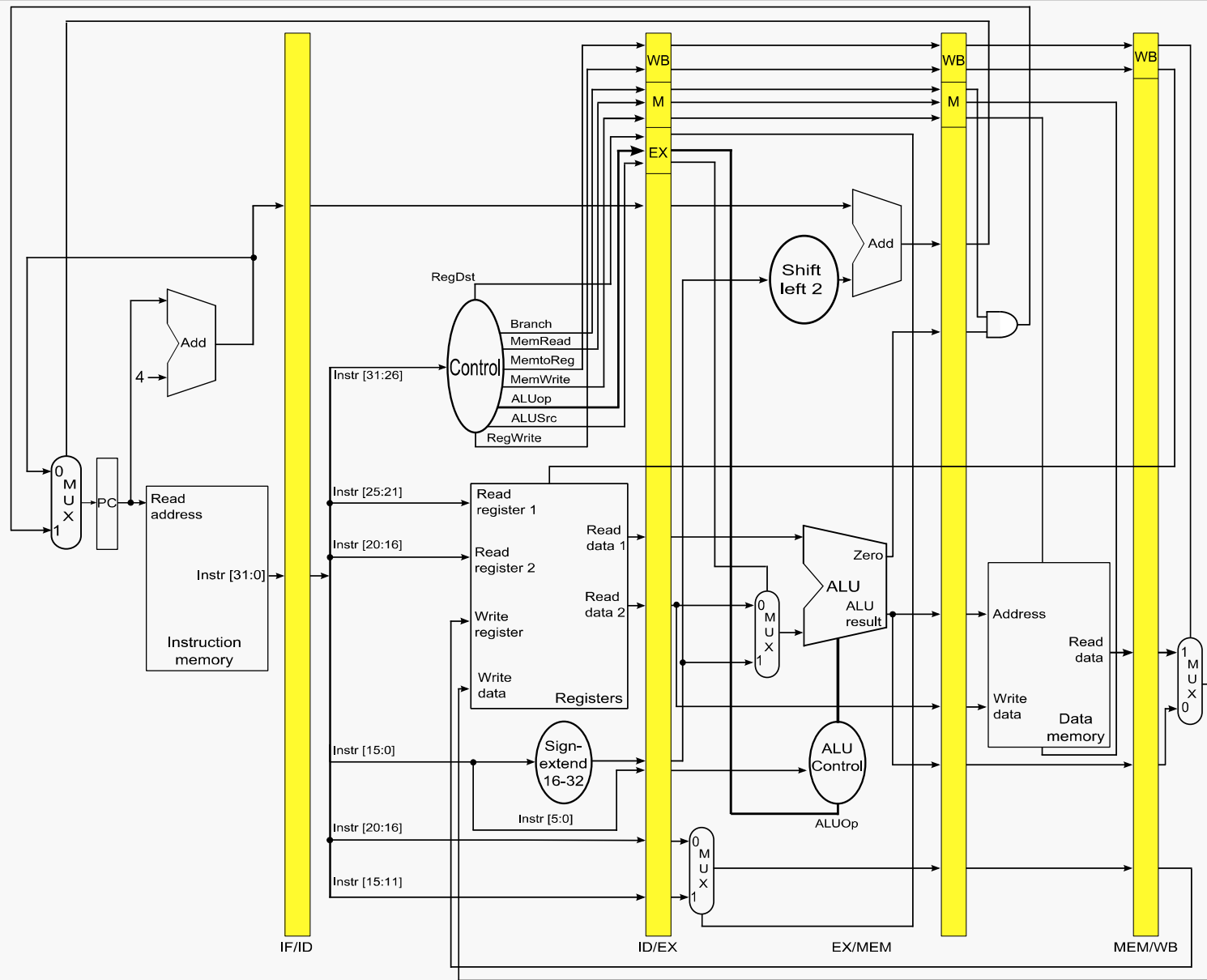

Consider this sequence:

```

 sub  $2, $1, $3    # value for $2 known end of EX stage;
                  # stored in $2 in WB stage
and  $12, $2, $5    # enters ID stage when sub enters EX;
                  # and needs $s2 when enters EX stage;
                  # sub is in MEM stage by then;
                  # $2 has not been written yet
    
```



| | | | | |
|---------|-----|-----|-----|-----|
| Tick 0: | sub | | | |
| Tick 1: | and | sub | | |
| Tick 2: | | and | sub | |
| Tick 3: | | | and | sub |

Data hazard?


Data Hazards in ALU Instructions

So this sequence leads to a data hazard involving \$2:

sub **\$2**, \$1, \$3

and \$12, **\$2**, \$5

 Can we resolve the hazard simply by forwarding?



Yes!

**But we must deliver the computed value at the right time; the next tick.
And, that value will be sitting in the EX/MEM interstage buffer.**

On the one hand, this is obvious. The first instruction writes a value into a register that is subsequently used as input by the second instruction:

```
sub  $2, $1, $3  
and  $12, $2, $5
```

We must know the register numbers for both instructions in order to detect the hazard.

More precisely, we must know rd for the first instruction and both rs and rt for the second instruction.

So, we must save those register numbers, via the interstage buffers.


Some notation will help us speak precisely about what's going on:

$B.RegisterRX$ = register number for RX sitting in interstage pipeline buffer B


A Glance Ahead

Pipeline Control 11

Passing the register numbers:

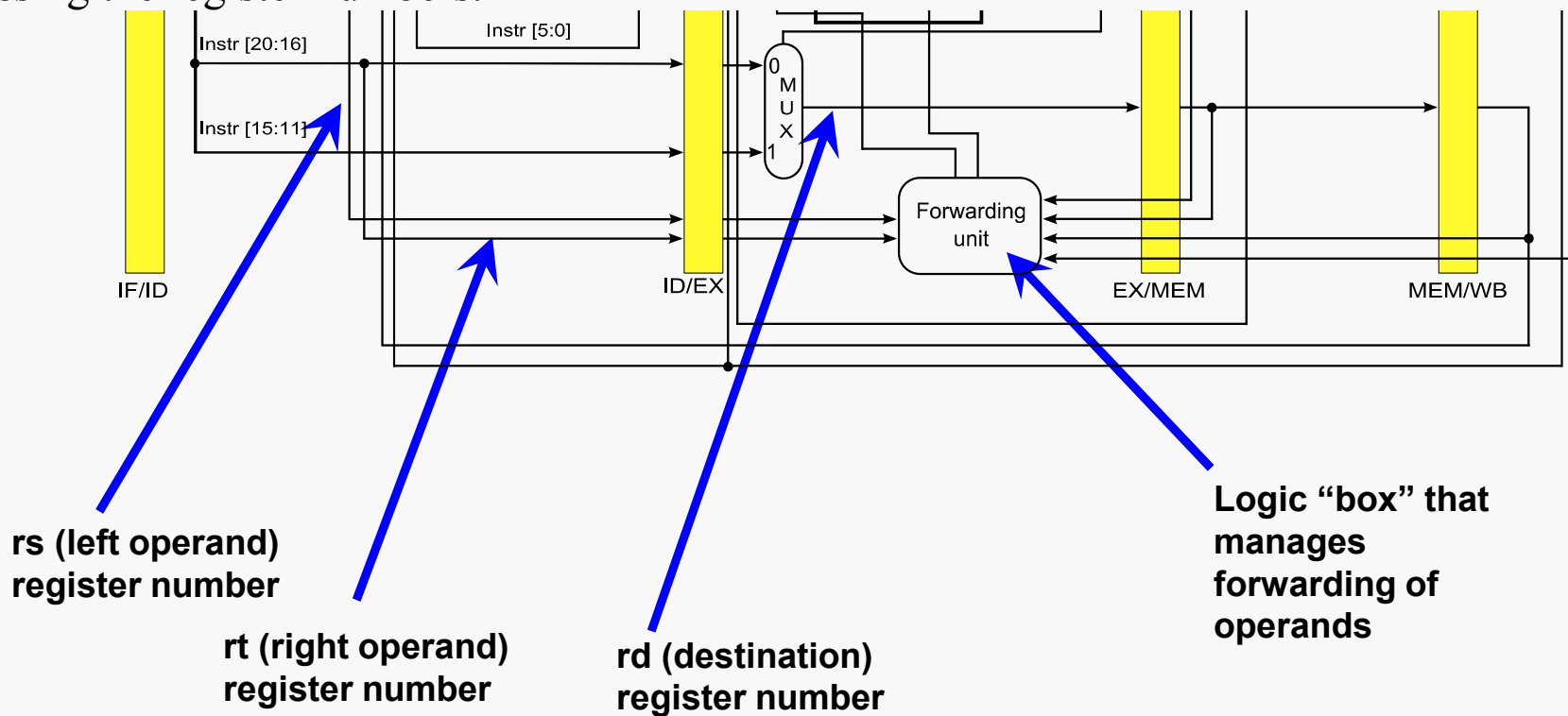

Passing the register numbers:

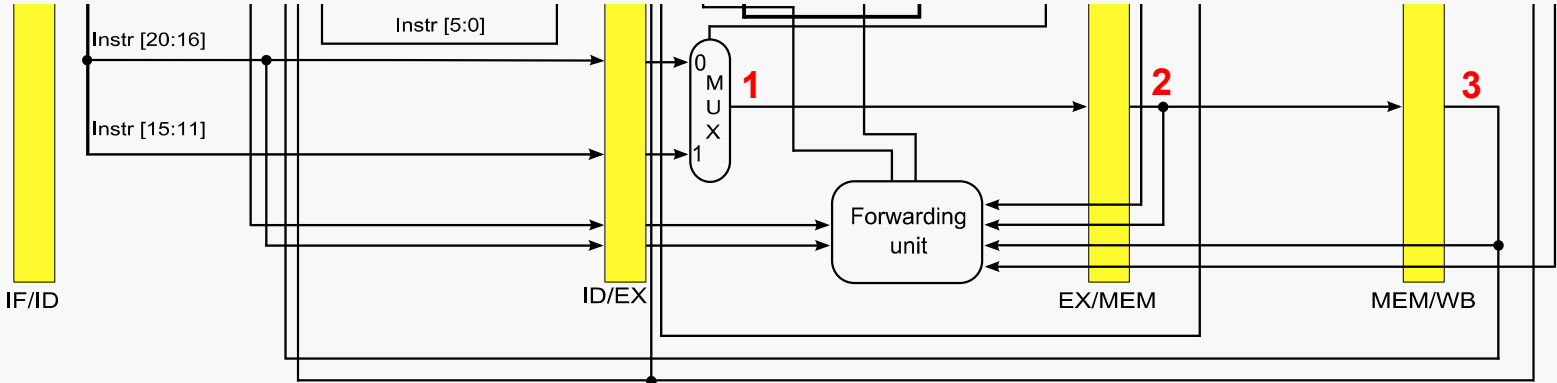

- 1:** rd for instruction currently in EX stage
- 2:** rd for instruction currently in MEM stage
- 3:** rd for instruction currently in WB stage

They may all be different!

Now, for this sequence of instructions:

```
sub    $2, $1, $3  
and    $12, $2, $5
```

So, we detect the hazard because we see that:

$$\text{EX/MEM.RegisterRd} == \text{ID/EX.RegisterRs}$$

Hence, we must forward the ALU output value from the EX/MEM interstage buffer to the `rs` input to the ALU.

Apparently, we'll need to:


- pass (at least some) register numbers forward via the interstage buffers
- add a logic unit to compare those register numbers to detect hazards
- add data connections to support transferring data values being forwarded
- add some more selection logic (multiplexors)

Data Hazards in ALU Instructions

Pipeline Control 14

Now, consider this sequence:
 
```
sub  $2, $1, $3    # value for $2 known in EX stage
and  $12, $2, $5    # enters ID stage when sub enters EX
or   $13, $6, $2    # enters ID stage when sub enters MEM;
                        # $2 has not been written yet
```




| | | | | | |
|---------|-----|-----|-----|-----|-----|
| Tick 0: | sub | | | | |
| Tick 1: | and | sub | | | |
| Tick 2: | or | and | sub | | |
| Tick 3: | | or | and | sub | |
| Tick 4: | | | or | and | sub |

Data hazard?

Again, we have a data hazard:
 
```
sub  $2, $1, $3    # value for $2 known in EX stage
and  $12, $2, $5    # enters ID stage when sub enters EX
or   $13, $6, $2    # enters ID stage when sub enters MEM;
```



| | | | | | |
|---------|-----|-----|-----|-----|-----|
| Tick 0: | sub | | | | |
| Tick 1: | and | sub | | | |
| Tick 2: | or | and | sub | | |
| Tick 3: | | or | and | sub | |
| Tick 4: | | | or | and | sub |

Yes!

Now, we must deliver the computed value after a delay of one tick, from MEM/WB.

Again, we have a data hazard:

```
sub  $2, $1, $3  
and  $12, $2, $5  
or   $13, $6, $2
```

So, we detect the hazard because we see that:

$$\text{MEM/WB.RegisterRd} == \text{ID/EX.RegisterRt}$$

Hence, we must forward the ALU output value from the MEM/WB interstage buffer to the rt^* input to the ALU.

So... detecting data hazards is a multi-stage affair.

*** QTP: why does this one go to the rt input?**


Data Hazards in ALU Instructions

Pipeline Control 17

Now, consider this sequence:

```
sub  $2, $1, $3    # value for $2 known in EX stage;
and  $12, $2, $5    # enters ID stage when sub enters EX;
or   $13, $6, $2    # enters ID stage when sub enters MEM;

 add  $14, $2, $2    # enters ID stage when sub enters WB;
                        # $2 has not been written yet, but. . .
```




| | | | | | |
|---------|-----|-----|-----|-----|-----|
| Tick 0: | sub | | | | |
| Tick 1: | and | sub | | | |
| Tick 2: | or | and | sub | | |
| Tick 3: | add | or | and | sub | |
| Tick 4: | | add | or | and | sub |

Data hazard?

Now, there's almost a hazard... but not quite...

```

 sub  $2, $1, $3    # value for $2 known in EX stage;
and  $12, $2, $5    # enters ID stage when sub enters EX;
or   $13, $6, $2    # enters ID stage when sub enters MEM;
add  $14, $2, $2    # enters ID stage when sub enters WB;
    
```



| | | | | | |
|---------|-----|-----|-----|-----|-----|
| Tick 0: | sub | | | | |
| Tick 1: | and | sub | | | |
| Tick 2: | or | and | sub | | |
| Tick 3: | add | or | and | sub | |
| Tick 4: | add | or | and | sub | sub |

Now, we deliver the computed value to the register file in the first half of tick 4, and it's not read until the second half of that tick!


Data Hazards in ALU Instructions

Pipeline Control 19

Now, consider this sequence:

```
sub  $2, $1, $3    # value for $2 known in EX stage;
and  $12, $2, $5    # enters ID stage when sub enters EX;
or   $13, $6, $2    # enters ID stage when sub enters MEM;
add  $14, $2, $2    # enters ID stage when sub enters WB

 sw   $15, 100($2)   # enters ID stage after sub is done
```



| | | | | | |
|---------|-----|-----|-----|-----|-----|
| Tick 0: | sub | | | | |
| Tick 1: | and | sub | | | |
| Tick 2: | or | and | sub | | |
| Tick 3: | add | or | and | sub | |
| Tick 4: | sw | add | or | and | sub |
| Tick 5: | | sw | add | or | and |

Data hazard?

Here's what we (seem to) know so far:

ALU-related data hazards occur when

EX/MEM.RegisterRd = ID/EX.RegisterRs
EX/MEM.RegisterRd = ID/EX.RegisterRt

Fwd from
EX/MEM
pipeline reg

MEM/WB.RegisterRd = ID/EX.RegisterRs
MEM/WB.RegisterRd = ID/EX.RegisterRt

Fwd from
MEM/WB
pipeline reg

However, we have overlooked (at least) one thing...

We don't need to forward unless the forwarding (earlier) instruction does actually write a value to a register:

EX/MEM.RegWrite == 1
MEM/WB.RegWrite == 1

And we only forward if Rd for that instruction is not `$zero`:

EX/MEM.RegisterRd != 0
MEM/WB.RegisterRd != 0

Datapath Change: ALU Operand Selection


Pipeline Control 22

Value from register fetch in ID stage

Value from WB stage


Value from ALU execution

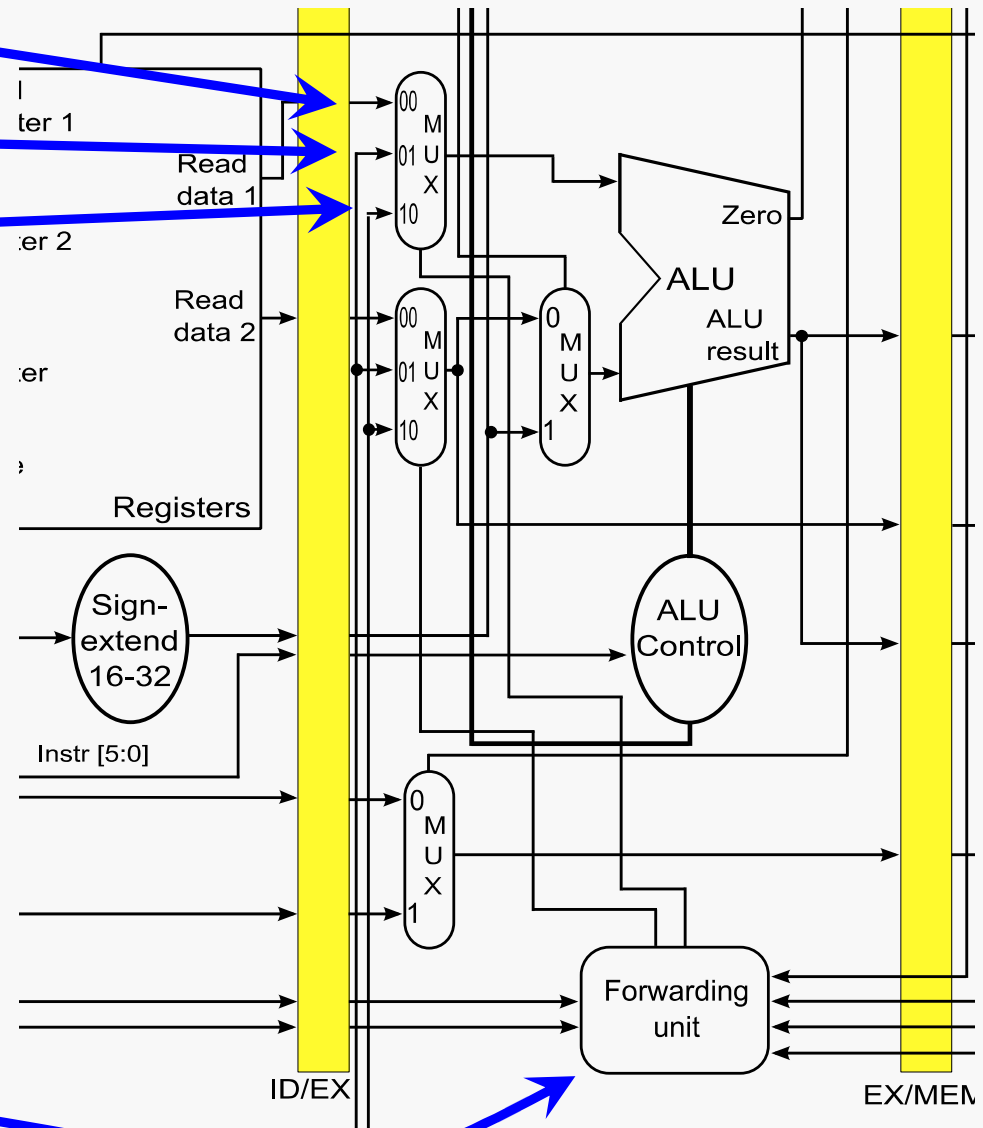Forwarding unit selects among three candidates for the register operands.



Forwarding Paths

Pipeline Control 23

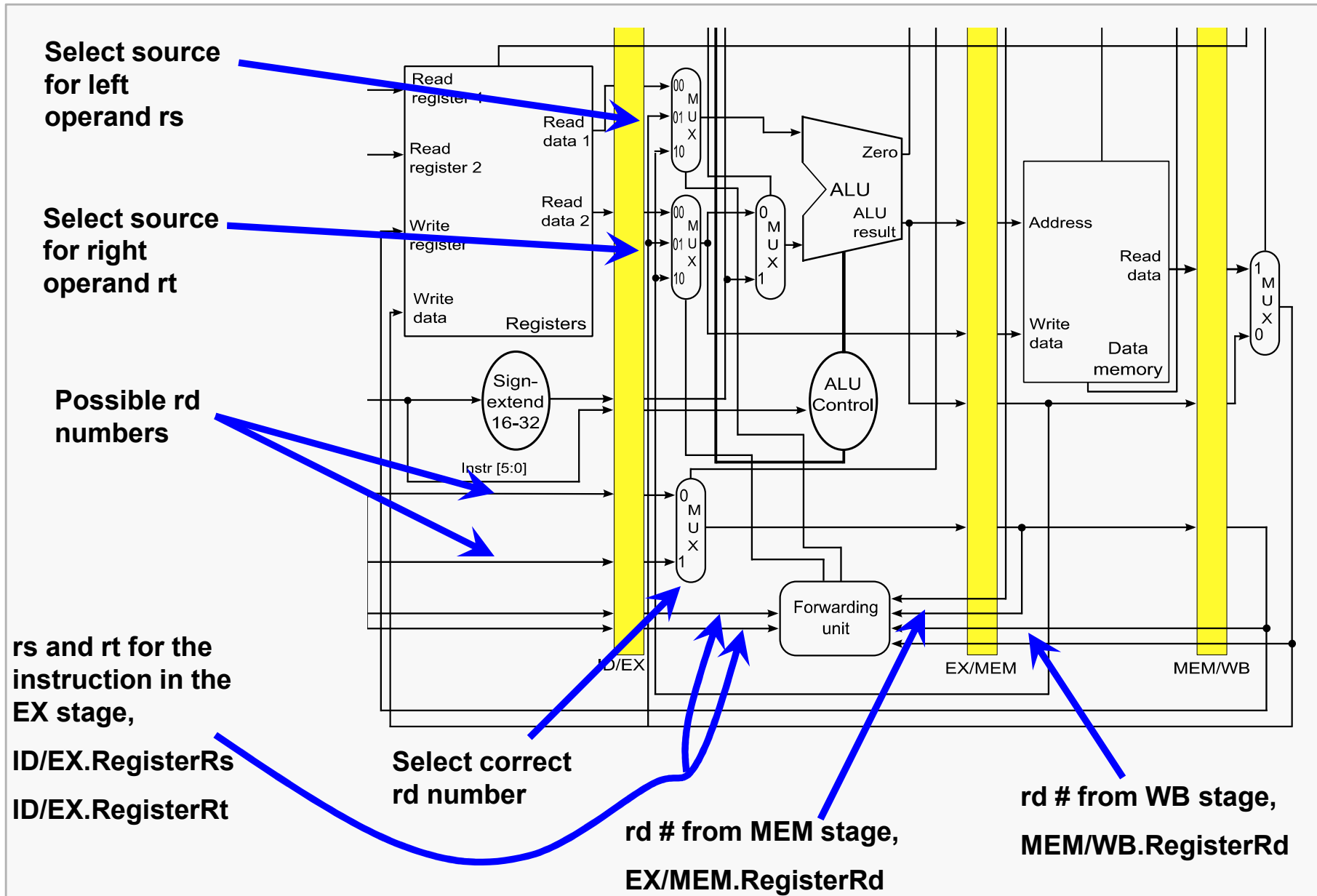

If (EX/MEM.RegWrite and
 EX/MEM.RegisterRd != 0 and
 EX/MEM.RegisterRd == ID/EX.RegisterRs)
then
 ForwardA = 10

Forwarding
unit

If (EX/MEM.RegWrite and
 EX/MEM.RegisterRd != 0 and
 EX/MEM.RegisterRd == ID/EX.RegisterRt)
then
 ForwardB = 10

**QTP: could BOTH occur with
respect to the same
instruction?**


```
If ( MEM/WB.RegWrite      and
      MEM/WB.RegisterRd != 0 and
      MEM/WB.RegisterRd == ID/EX.RegisterRs )
```

then

ForwardA = 01

```
If ( MEM/WB.RegWrite      and
      MEM/WB.RegisterRd != 0 and
      MEM/WB.RegisterRd == ID/EX.RegisterRt )
```

then

ForwardB = 01


**QTP: could BOTH an EX hazard and a
MEM hazard occur with respect
to the same instruction?**

Consider the sequence:

add **\$1**, \$1, \$2

add **\$1**, **\$1**, \$3

add \$1, **\$1**, \$4

 

Both hazards occur... which value do we want to forward?

Revise MEM hazard condition:

- Only forward if EX hazard condition is not true


Forwarding
unit

If (MEM/WB.RegWrite and
MEM/WB.RegisterRd != 0 and
not (EX/MEM.RegWrite and
EX/MEM.RegisterRd != 0 and
EX/MEM.RegisterRd == ID/EX.RegisterRs) and
MEM/WB.RegisterRd == ID/EX.RegisterRs)
then
ForwardA = 01

If (MEM/WB.RegWrite and
MEM/WB.RegisterRd != 0 and
not (EX/MEM.RegWrite and
EX/MEM.RegisterRd != 0 and
EX/MEM.RegisterRd == ID/EX.RegisterRt) and
MEM/WB.RegisterRd == ID/EX.RegisterRt)
then
ForwardB = 01

Simplified Datapath with Forwarding

Pipeline Control 28

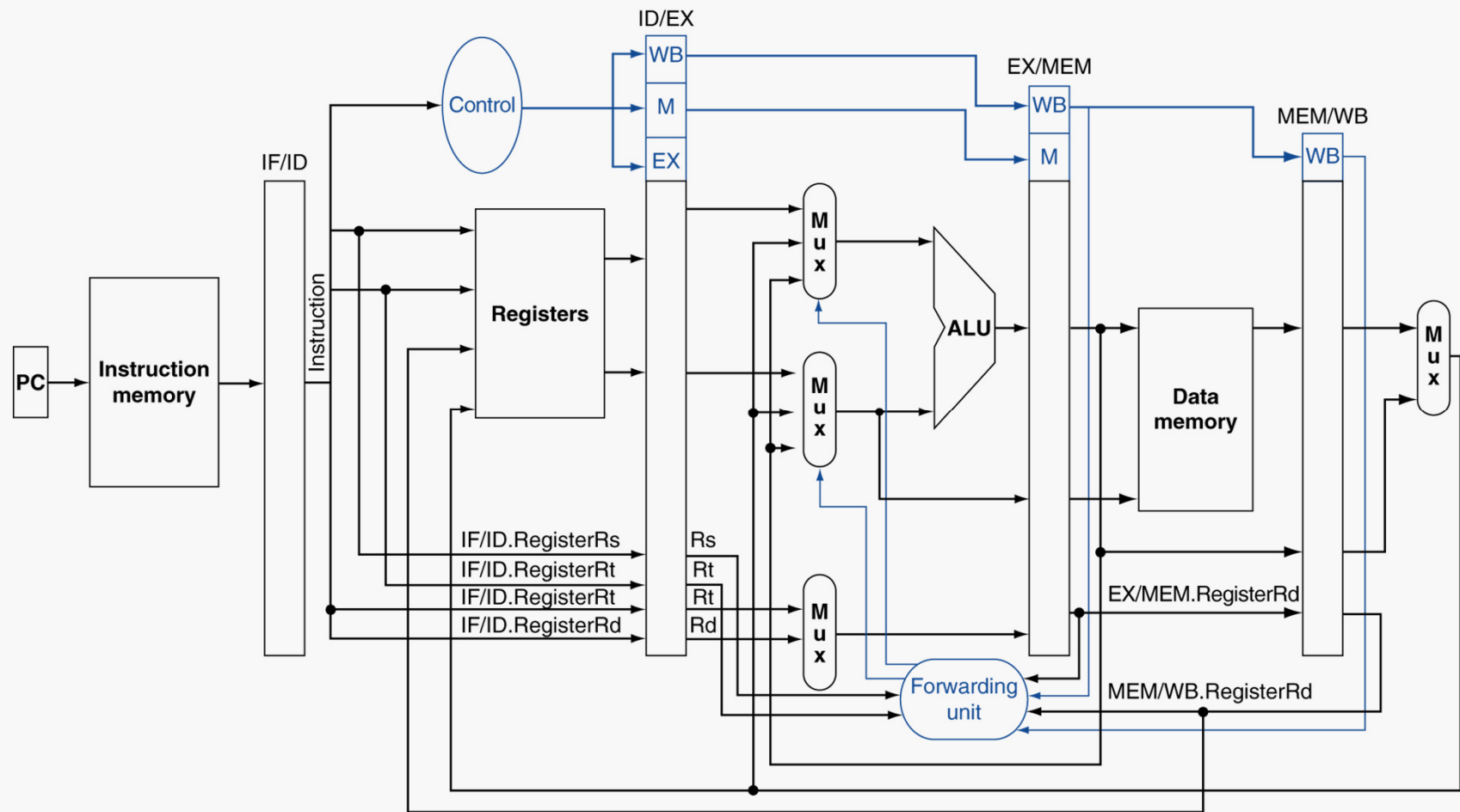

Unsimplified Datapath with Forwarding

Pipeline Control 29

